



[Home](#) » [Tutorials](#) » [Synchronous Logic](#)

# Synchronous Logic

2024-09-17 · 16 min · Justin Rajewski | [Suggest Changes](#)

► [Table of Contents](#)

In this tutorial you will be introduced to the *D flip-flop* and how you can use these to make an LED blink.

## Digital Design Fundamentals



Synchronous logic is a fundamental building block for just about any digital design. It allows you to create much more complex systems that accomplish something over a



series of steps. It also gives you the ability to save states and other information.

# The Problem

In our last tutorial we simply wired an LED to a button. Whenever you pressed the button the LED would turn on. Our design had no concept of time. The goal for this project is to blink an LED. That means we have to create a circuit that can turn itself on and off automatically after a regular interval of time has passed. For this we need the flip-flop.

# Clocks

Before I can explain what exactly a flip-flop does, you need to understand what a clock is.

A clock is just a signal that toggles between 0 and 1 over and over again. It looks something like this.

The important thing is the rate at which it toggles. The Alchitry boards have a 100MHz clock. That means that it toggles 100 million times per second!

The clock has two edges, the *rising edge* and the *falling edge*. I drew the rising edges with little arrows. It is when the clock transitions from 0 to 1. The rising edge is usually the important one.



# D Flip-Flops

This is one of the most important circuit elements you will be using. Lucky for you, it is also fairly straightforward how they work. Take a look at the symbol for the flip-flop below.

This image shows all the signals that a flip-flop could have, but in practice, the only required signals are  $D$ ,  $Q$ , and  $clk$ .

So what exactly does this thing do? All it does is copy the signal at  $D$  to  $Q$  whenever there is a rising edge on the  $clk$  input. That means  $Q$  will keep its value between rising edges of the clock. Since the flip-flop *remembers* what the input was at  $D$ , it is actually one of the most basic memory elements.

## Loops

Let's take a look at the following example.

What will this circuit do? If the input to the gate is 1, then its output is 0. However, the output is the input so the output must be 1, but then the input is 1 so the output



must be 0? If we assume that the signal can only be 0 or 1 it seems like it would toggle between 0 and 1 infinitely fast. In practice, remember that signals are actually represented by voltages, it may oscillate, or it may settle to somewhere in the middle. This is, of course, something we don't want. Designing circuits with feedback can be very tricky to make sure something like this doesn't happen and that the circuit will work how you expect it to.

That is why we don't! Instead, we use a circuit like this one.

What will this circuit do? Well, for now let's just assume that  $Q$  is 0. That means that  $D$  is 1 (because it went through the not gate). On the next rising edge of the clock  $Q$  will copy what  $D$  is, so  $Q$  becomes 1. Once  $Q$  becomes 1,  $D$  becomes 0. You can follow the pattern to realize that every time there is a rising edge on the clock the output of the flip-flop toggles.

What about the initial condition though? If we just built this circuit how do we know if  $Q$  is 0 or 1? The truth is that we don't and in some cases it may be 1 while others it may be 0. That is where the *rst* signal comes in. This signal is used to reset the flip-flop to a known state. In FPGAs this signal is generally very flexible and allows you to reset the flip-flop to a 1 or 0 when the signal is high or low (your choice, not both).



Lucid, `dff` uses active high resets. That means when the `rst` signal is `1`, the flip-flop is held in reset.

There are cases where you don't care what the initial value of the flip-flop is, in those cases you don't need to, and shouldn't, use a reset.


Since the only signal left is `en`, I'll cover it now just for completeness. There are times when you want the flip-flop to ignore the rising edges on the clock and to preserve the contents of `Q`. That is when you use the `enable` signal. When the `en` signal is `1`, the flip-flop operates normally. When it is `0` the contents of `Q` won't change on the rising edges of the clock. If you see a flip-flop without an `en` signal it is just assumed that the flip-flop is always enabled.

In Lucid, `dff` doesn't have an explicit `en` signal. However, they will retain their value if you don't write something new to it.

 
## Creating the Module

Open Alchitry Labs and create a new project based on the *Base Project*. I'm going to call mine *BlinkerDemo*.

With the new project open, click the *New File* icon (the second left most icon in the toolbar) and choose *New Lucid Module*. In the dialog that open, enter `blinker` as the module name and click *Create*.



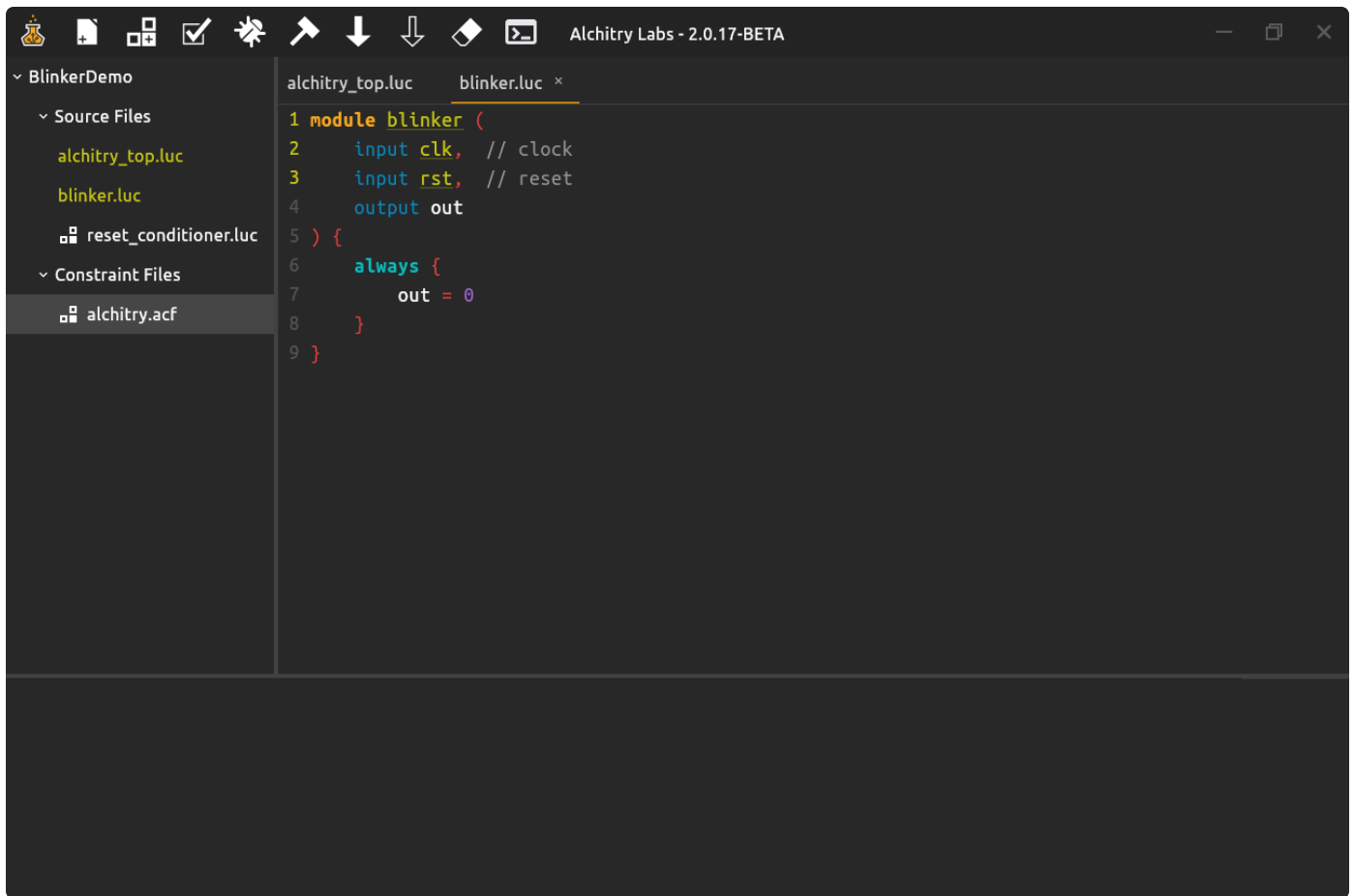The file should now be under *Source Files* in the project tree, and it should automatically open.



# Writing the Blinker

Edit the module so that it looks like the following.

```
1 module blinker (  
2     input clk, // clock  
3     input rst, // reset  
4     output blink // output to LED  
5 ) {  
6  
7     dff counter[25](.clk(clk), .rst(rst))  
8  
9     always {  
10         blink = counter.q[24]  
11         counter.d = counter.q + 1  
12     }
```



13 }

Let's go over what changes were made. First, I simply renamed `out` to `blink` to better reflect what our module does.

Line 7 has the declaration of the flip-flop. Lucid has a type `dff` for creating flip-flops. The flip-flop I created is called `counter` and it's 25 bits wide.

I then connected the `clk` signal of our module to the `clk` input of the flip-flop. I did the same with the `rst` signal. The syntax for connecting these signals is `.port_name(signal)` where `port_name` is the name of the port on the module and `signal` is the signal to connect to it. In this case the module input and signal names are the same.

In the `always` block, line 10 simply connects our output, `blink`, to the most significant bit of `counter.q`. When you are working with flip-flops or module instances, you use the dot syntax to specify which signal you want. In this case, we need to read the `q` output of the `dff` so we use `counter.q`.

The next line connects the input, `d`, of the `dff` to its output, `q`, plus one. This means that every time `clk` goes high, `counter.q` will increase by 1.

When instantiating a `dff`, you must connect its `clk` input and optionally `rst` input. These can't be connected later in an `always` block.

## Reset

Notice we connect the `rst` signal to the counter. What does this do? Whenever the `rst` signal goes high, the value of `counter.q` becomes 0. This is also the value that the counter is initialized to when the FPGA first starts.

If we wanted the counter to initialize and reset to a different value, we can specify the value using the `dff` parameter `#INIT`.

```
dff counter[25](#INIT(100), .clk(clk), .rst(rst))
```

The counter will now start with a value of 100 and reset to 100. Zero is the default value if none is specified.

Notice that parameters are specified with `#NAME` instead of `.name`. Parameter names are always fully capitalized.

If you don't need to reset a `dff` for some reason, you can simply not connect anything to the `rst` input, and it won't have a reset. This is recommended if you don't need a reset since it doesn't force the tools to route the reset signal to the flip-flop.

The `dff` type is special in that the `rst` input is optional. All other inputs and all inputs to modules are required.

## The Counter

Here is what the counter circuit looks like. Keep in mind that there is actually 25 flip-flops (but only one +1 circuit) and the connections are actually 25 wires, or bits, wide. When many flip-flops are used to store a single multi-bit value they are commonly drawn as a single flip-flop.





Let's look at what this module will actually do. Right after the `rst` signal goes low, `counter.q` will be 0. That means that `counter.d` will be 1, since our combinational block assigns it `counter.q` plus 1.

At the next positive edge of `clk`, `counter.q` will be assigned the value of `counter.d`, or 1. Once `counter.q` is 1, `counter.d` must be 2. You should be able to see what will continue to happen. Each clock cycle, `counter.q` will increase by 1. But what happens when `counter.q` is `25b11111111111111111111111111111111` (the max value)?

Since we are adding a 1 bit number to a 25 bit number, the result can be up to 26 bits, but since we are storing it into a 25 bit `dff` we lose the last bit. That means that when `counter.q` is the max value, `counter.d` is 0 and the process starts all over again.

Our counter will continuously count from 0 to 33554431 ( $2^{25} - 1$ ).

How do we make an LED blink from this counter? It's simple once you realize that for half the time the most significant bit is 1 and the other half of the time it's 0. This is because if `counter.q` is less than 16777216 ( $2^{24}$ ), then the 24th bit must be 0 and when it is equal or greater, the MSB must be 1. That means we can just connect the LED to the most significant bit of our counter. If you need to convince yourself this is true try writing out the binary values from 0-7 and look at how the MSB (most significant bit) changes.

How fast will the LED blink though? We know that the clock frequency is 100MHz, or 100,000,000 clock cycles per second. Since our counter takes  $2^{25}$  cycles to overflow we can calculate the blinker time,  $2^{25} / 100,000,000$  or about 0.34 seconds. The LED will turn on and off every 0.34 seconds. If you wanted to make that time longer, you can just make the counter 26 bits long and the time will double to 0.67 seconds. If you wanted to make it blink faster you can make the counter shorter.

## Module connections



In Lucid, there are three ways to specify an input to a module or `dff` . The first way is how we did it in this example.

```
dff counter[25](.clk(clk), .rst(rst))
```

Here we specify the connections in a set of parentheses directly after the name. These connections are only applied to this single module. However, we can use the next method to make the same connections to many modules.

```
.clk(clk), .rst(rst) {  
    dff counter1[12]  
    dff counter2[7]  
    dff counter3[8]  
}
```

In this example, we connect the `clk` and `rst` inputs of all the modules contained in the curly braces. In this case, they contain three `dffs` . This is convenient since most modules will require a clock and reset signal.

You can also nest this method.

```
.clk(clk) {  
    .rst(rst) {  
        dff counter1[12]  
        dff counter2[7]  
    }  
    dff counter3[8]  
}
```

Here only `counter1` and `counter2` are connected to `rst` .

You can also mix this method with the first.

```
.clk(clk) {  
    dff counter1[12](.rst(rst))
```



```

dff counter2[7]
dff counter3[8]
}

```

Here only `counter1` is connected to `rst` .

Finally, the last way to specify an input is simply by not connecting it when declaring the module but rather inside an always block later. This is what we did with `counter.d` . Note that `dff` requires you to specify `clk` and `rst` when instantiating them, and they do not allow you to specify the `d` input then.

When connecting an array of module instances, there is a difference when connecting an input directly or in a connection block. Connections to module arrays made directly connect to the array as a whole. Connections made with a connection block are connected to each individual instance.

This allows you to easily specify a clock to be distributed to all instances but still connect up unique values directly. See [the reference guide](#) for more details.

If you specify an input in an always block, you can specify the input to each element separately. In this example, the `clk` signal is one bit, but it is getting copied to 25 one bit flip-flops. However, the `d` input, which is also one bit, is packed into a 25 bit array to use in the always block. That way we can use the `d` input as if it is really one big flip-flop (which don't actually exist).

## Instantiating a module

Now that we have a blinker module we need to add it to our top level module.

Open up the top file and make the edits so it looks the same as below.

```

1 module alchitry_top (
2     input clk,           // 100MHz clock
3     input rst_n,         // reset button (active low)

```



```

4      output led[8],           // 8 user controllable LEDs
5      input  usb_rx,          // USB->Serial input
6      output usb_tx           // USB->Serial output
7  ) {
8
9      sig rst                  // reset signal
10
11      .clk(clk) {
12          // The reset conditioner is used to synchronize the reset sig
13          // clock. This ensures the entire FPGA comes out of reset at
14          reset_conditioner reset_cond
15
16          .rst(rst) {
17              blinker my_blinker
18          }
19      }
20
21      always {
22          reset_cond.in = ~rst_n    // input raw inverted reset signal
23          rst = reset_cond.out      // conditioned reset
24
25          led = 8x{my_blinker.blink} // blink LEDs
26
27          usb_tx = usb_rx           // echo the serial data
28      }

```

In the nested `.clk(clk)` and `.rst(rst)` blocks, I instantiated the blinker module and named it `my_blinker`. Notice I'm using the batch way of connecting the `clk` and `rst` inputs this time. This is because you will likely want to add more modules to your top level module so it can be nice to set it up beforehand.

In the `always` block, we connect the `blink` output of `my_blinker` to the eight LEDs using the duplication syntax covered in the previous tutorial.



You should now be able to build and load the project. All 8 LEDs should blink about two times per second.

# Simulation

If you try and simulate this code, it will likely seem like it isn't working.

This is because the simulation clock runs at 1KHz by default. With a 25 bit counter, it will take 4.7 hours for the LED to turn on.

If we change the counter to 9 bits instead, it'll take only half a second to blink.

```
module blinker (  
    input clk,    // clock  
    input rst,    // reset  
    output blink // output to LED  
) {  
  
    dff counter[9](.clk(clk), .rst(rst))  
  
    always {  
        blink = counter.q[8]  
        counter.d = counter.q + 1  
    }  
}
```

We can clean this up using the `$is_sim()` function. This function evaluates to `1` if you are running an interactive simulation, and `0` otherwise.

Using this and the ternary operator we can update the code to work in both cases.

```
module blinker (  
    input clk,    // clock  
    input rst,    // reset
```



```

    output blink // output to LED
) {

    dff counter[$is_sim() ? 9 : 25](.clk(clk), .rst(rst))

    always {
        blink = counter.q[$is_sim() ? 8 : 24]
        counter.d = counter.q + 1
    }
}

```

The ternary operator looks like `condition ? when_true : when_false`. When `condition` is *true* (meaning non-zero), the value of the operator is `when_true`. Otherwise, it is `when_false`.

## Width Function

We can actually simplify this a bit more. It is very common to want to index something based on the width of the signal. For that, and other cases, we have the `$width()` function.

The `$width()` function takes any signal as an argument and returns its width. See the [reference page](#) for more details.

We can rewrite the indexing of the MSB of `counter.q` from `counter.q[$is_sim() ? 8 : 24]` to `counter.q[$width(counter.q) - 1]`. This way no matter what size `counter.q` is, we will always be indexing the last bit.

## The Reset Conditioner

Now that we have actually used the reset signal for what it was intended for, we talk about the `reset_conditioner` module. The signal `rst_n` comes from outside the FPGA. Signals from outside the FPGA are UNCLEAN!

What I mean by this is that we don't know how external signals (especially from a button) will change in relation to the clock we are using. If the reset signal goes low really close to the rising edge of the clock, due to internal delays in the FPGA, some flip-flops may come out of reset before the rising edge while others could after. This means some flip-flops may stay reset for a cycle longer than others (NOT GOOD). Even worse, when signals change too close to a rising edge of a clock you run into metastability issues. This is covered later, but it basically means you aren't guaranteed the output of the flip-flop will be 1 or 0. It could be somewhere in between (0.5?) or even oscillate between values (BAD).

This is where the reset conditioner comes in. It is a fairly simple circuit that synchronizes the reset signal to the FPGA's clock. This ensures that your entire design will come out of reset at once. If you want to read more than you'll ever want to know about resets, check out [this paper from Xilinx](#).

« PREV

NEXT »

[Your First FPGA Project](#)[Io Element](#)© 2025 [Alchitry](#)